

# Midterm Exam

600.229 Computer Systems Fundamentals

Spring 2018

Johns Hopkins University

Instructor: Prof. Philipp Koehn

9 March 2018

Complete all questions.

Use additional paper if needed.

Time: 50 minutes.


Name of student:

Solution (corrected)

### Q1. Analysis of Circuit

25 points

Consider the following circuit:

 

Assume that at the onset, the wires are activated as follows:  $A=1, B=1, C=1, D=0$ .

Moreover, assume that it takes 1ms for a NAND gate to change its output value.

The following actions are performed:

- At time 10ms, the key connected to wire (B) is opened.
- At time 20ms, the key connected to wire (B) is closed.
- At time 30ms, the key connected to wire (A) is opened.
- At time 40ms, the key connected to wire (A) is closed.

Trace the activation levels for each wire (A)–(D) at each time step when wire activations change values.




## Q2. Design a Circuit

25 points

You are given the following truth table for a function.

A	B	C	OUT
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

 Design a circuit with AND, OR, and NOT gates that implements this function (hint: use CNF or DNF).





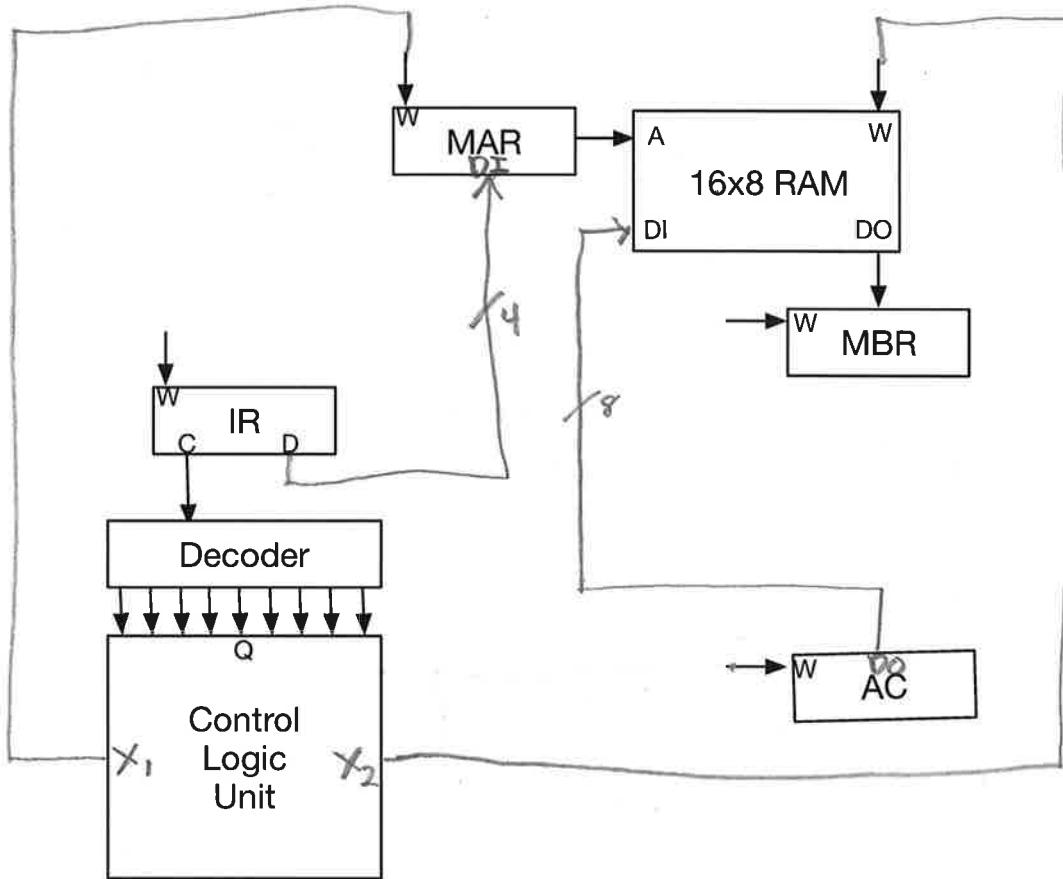
### Q3. SCRAM Circuit

25 points

Below is an incomplete diagram of a SCRAM circuit (consisting of IR = Instruction Register, MAR = Memory Access Register, MBR = Memory Buffer Register, and AC = accumulator).



Design the STA command (storing a value from the accumulator into memory)

1. Add all the required control signal from the control logic unit and wiring to the diagram (you do not add anything inside the control logic unit).
2. Write the micro-program that implements the STA command (you do not write micro-code for the instruction fetch).

Assume  $t_3$  indicates STA

$t_3 q_3 : \text{MAR} \leftarrow \text{IR}(D)$        $(x_1)$   
 $t_4 q_3 : \text{M} \leftarrow \text{AC}; \text{END}$        $(x_2)$

$t_0 - t_2$  are steps for instruction fetch

6

↑  
reset timer to start instruction fetch for next instruction



### Q4. SCRAM Code


25 points

Consider the following code of a SCRAM-like program.

Address	Operation	Data	Time	PC	M[13]	M[14]	M[15]	A
	LDA		0	0	3	0	0	3
0	LDA	13	1	1	3	3	0	3
1	STA	14	2	2	2	3	0	3
2	DEC	13	3	3	2	3	0	3
3	JPZ	11	4	4	2	3	0	2
4	LDA	13	5	5	2	3	2	2
5	STA	15	6	6	2	3	2	3
6	LDA	14	7	7	2	3	1	3
7	DEC	15	8	8	2	3	1	3
8	JPZ	1	9	9	2	3	1	6
9	ADD	14	10	10	2	3	1	6
10	JMP	7	11	7	2	3	0	6
11	PRINT	14	12	1	2	6	0	6
12	HLT		13	2	1	6	0	6
13	DAT	3	14	3	1	6	0	6
14	DAT	0	15	4	1	6	0	1
15	DAT	0	16	5	1	6	1	1
	LDA		17	6	1	6	1	6
	DEC		18	7	1	6	0	6
	JPZ		19	8	1	6	0	6
	STA		20	1	1	6	0	6
	DEC		21	2	0	6	0	6
	JPZ		22	3	0	6	0	6
	PRINT		23	11	0	6	0	6
	HLT		24	12	0	6	0	6

Operations:

 - STA: store accumulator
- LDA: load accumulator
- ADD: add to accumulator
- DEC: decrement the value at memory address
- JMP: jump to memory address
- JPZ: jump to memory address if last DEC resulted in 0
- DAT: dummy instruction (data value used only)
- PRINT: print value at memory address



What is the number printed by the program?

Show your work (for instance by reporting values in relevant memory locations).





